

Spice model makes it easy to design with PWM amplifiers

YU JEN WONG, APEX MICROTECHNOLOGY CORP

The recent availability of high-voltage and high-current PWM amplifiers in hybrid packages has attracted the interest of many designers who traditionally use linear amplifiers. The advantage of PWM amplifiers is obvious: efficiency of 70 to 97%. High efficiency translates to lower internal power loss, smaller heat sinks, and reduced overall physical size.

To make it easier to design with these amplifiers, a simple and versatile generic PWM Spice model lets you check out


High-efficiency PWM amplifiers are displacing linear designs in many applications. You can design a constant-current or a constant-voltage PWM amplifier with the aid of a simple yet versatile Spice model.

PWM waveforms without the fear of blowing up the amplifiers or getting shocked by high voltages. The methodology behind generating such a model applies not only to hybrid PWM amplifiers, but also to monolithic and discrete PWM amplifiers. The inputs to the

model come from the PWM amplifier's data sheet, and you can run the model on any commercial Spice program.

Even though a PWM amplifier offers analog signals in and analog signals out, its circuit functionality is entirely differ-

FIGURE 1

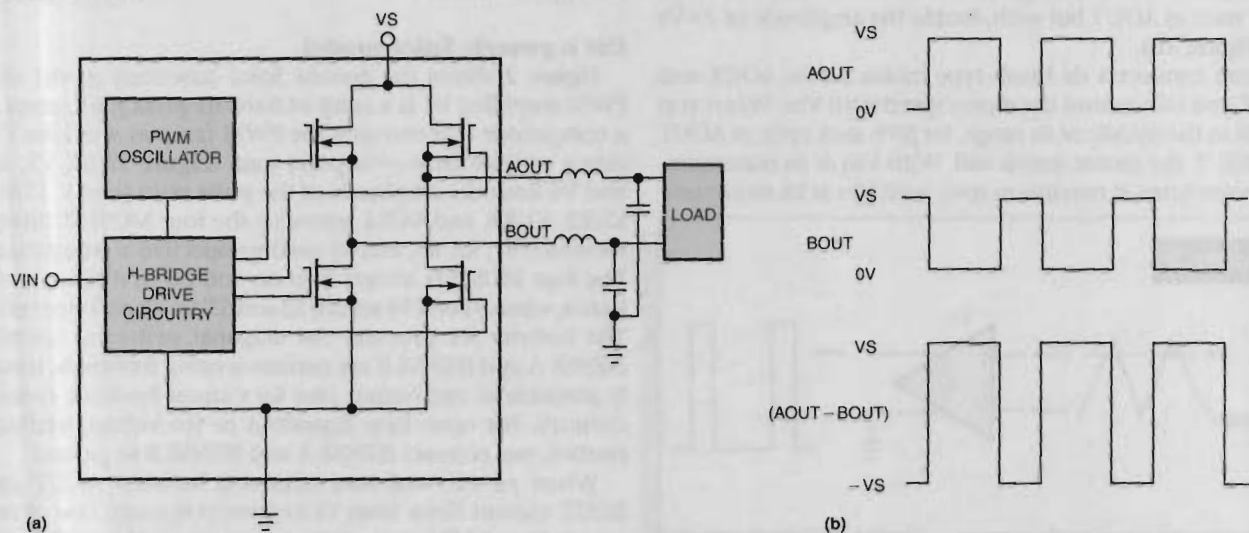

A PWM amplifier (a) converts an analog signal into a pulse train of variable duty cycle (b). AOUT and BOUT can directly drive a dc motor, but most other loads require additional LC filtering.

PWM AMPLIFIERS

ent from a linear amplifier's. A PWM amplifier modulates a pulse train in the time domain and uses LC filtering to extract the analog-signal output. You can use PWM amplifiers to emulate linear constant-voltage amplifiers or linear constant-current amplifiers, both at much higher levels of efficiency.


If you're unfamiliar with how a PWM amplifier works, you're not alone. Just like op amps, PWM amplifiers come in many sizes and flavors, some with fancy bells and whistles. Fortunately, the amplifiers all operate under the same principle.

A PWM amplifier converts an analog signal into a pulse train of variable duty cycle. The analog input controls the duty cycle of the output pulse train, which switches on and off once during each cycle. When a high output is necessary, the pulse train switches on most of the time and vice versa.

Figure 1a shows a basic PWM amplifier. V_{in} is the analog input of 1 to 8V dc. AOUP is a pulse train, and BOUP is its inverse. The PWM oscillator determines the frequency of the pulse train, and some PWM amplifiers allow you to put in your own PWM oscillator. As V_{in} changes from its minimum to its maximum value, the duty cycle of AOUP changes from 0 to 100%, and the duty cycle of BOUP changes from 100 to 0%. The difference voltage of AOUP-BOUP has the same pulse train as AOUP but with double the amplitude of $2 \times V_s$ p-p (Figure 1b).

If you connect a dc brush-type motor across AOUP and BOUP, you can control the motor speed with V_{in} . When you set V_{in} in the middle of its range, for 50% duty cycle at AOUP and BOUP, the motor stands still. With V_{in} at its maximum, the motor turns at maximum rpm; with V_{in} at its minimum,

FIGURE 2

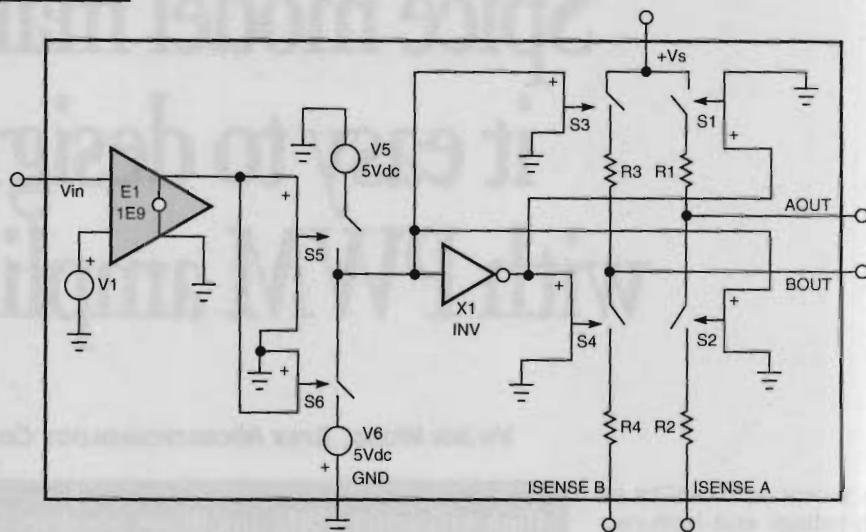

A generic Spice model of a PWM amplifier includes a fixed-frequency ramp (V1), a comparator (E1), an inverter (X1), and MOSFET drivers (S1 to S4) and their respective on-resistances (R1 to R4).


the motor reverses direction of rotation and turns at maximum rpm again. You can directly connect AOUP and BOUP to a motor because the winding inductance of the motor turns the pulsed voltage into a rippled dc current whose magnitude controls the motor speed and whose polarity controls the clockwise or counterclockwise direction of the motor. As Figure 1a indicates, most other applications need LC filters to filter out the PWM pulse train to ensure that an analog signal appears at the load.

Use a generic Spice model

Figure 2 shows the generic Spice subcircuit model of a PWM amplifier. V1 is a ramp of fixed frequency. E1 serves as a comparator that converts the PWM ramp as it crosses V_{in} into a variable-duty-cycle pulse train (Figure 3). S5, V5, S6, and V6 limit the amplitude of the pulse train to $\pm 5V$. S1/R1, S2/R2, S3/R3, and S4/R4 represent the four MOSFET drivers for which R1, R2, R3, and R4 are the respective on-resistances. The four MOSFETs always turn on and off in diagonal sets, that is, when S1 and S4 are on, S2 and S3 are off and vice versa. The inverter X1 provides the diagonal switching control. ISENSE A and ISENSE B are current-sensing terminals, usually available at two output pins for current-feedback control circuitry. For open-loop operation or for voltage-feedback control, just connect ISENSE A and ISENSE B to ground.

When an external load connects between AOUP and BOUP, current flows from V_s to ground through one of two routes: V_s to S1/R1, to an externally connected load between AOUP and BOUP, to S4/R4, and then to ground or V_s to S3/R3, to the external load, to S2/R2, and finally to ground. The voltage across the load actually doubles the V_s voltage.

FIGURE 3

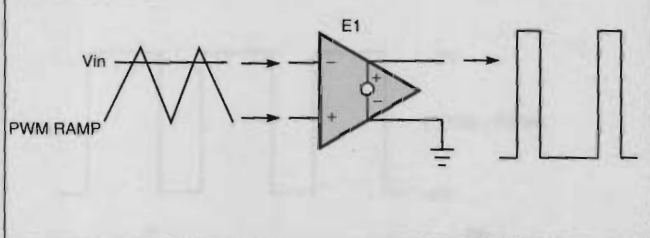

In the PWM-amplifier model, E1 serves as a comparator that converts the PWM ramp as it crosses V_{in} into a variable-duty-cycle pulse train.

PWM AMPLIFIERS

For example, when $V_s=100V$, the voltage across the load is 200V p-p. This voltage-doubling feature is another advantage PWM amplifiers offer for high-voltage applications. To double voltage using linear amplifiers you must use two linear amplifiers in a bridge-mode configuration.

Design example: constant-current amplifier

You commonly use constant-current amplifiers for applications such as motor-torque control and battery chargers. You can use the model and the specifications of a commercial PWM amplifier—in this case, the Apex (www.apexmicrotech.com) SA50—to design a constant-current amplifier (also called a voltage-to-current converter). You start out with the following specifications from the SA50 data sheet:

Analog input voltage/output duty cycles:

$V_{in}=4V$; AOUT=0% and BOUT=100%


$V_{in}=6V$; AOUT=50% and BOUT=50%

$V_{in}=8V$; AOUT=100% and BOUT=0%


switching frequency: 45 kHz.

MOSFET on-resistance: 0.5Ω total or 0.25Ω each

The analog input voltage range of 4 to 8V dc and the

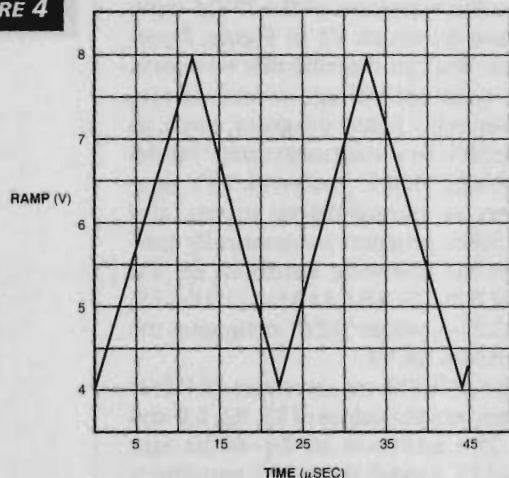FIGURE 4

The analog input-voltage range and the switching frequency (in this case, 4 to 8V and 45 kHz, respectively) determine the waveform of the PWM ramp.

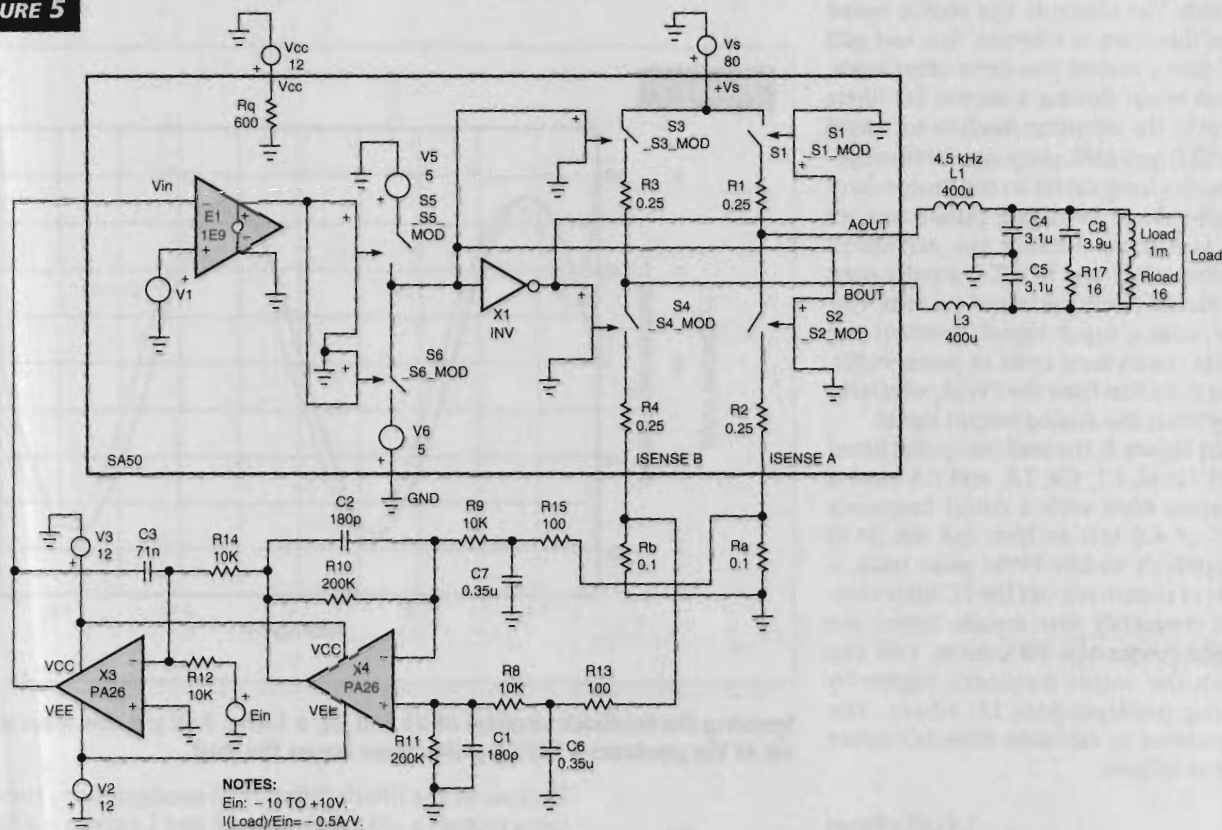FIGURE 5

Combining the generic Spice model with the specifications for the SA50 PWM amplifier, you can use the model to simulate a voltage-controlled, constant-current amplifier

PWM AMPLIFIERS

switching frequency of 45 kHz determine the waveform of the PWM ramp (Figure 4), which V1 in Figure 2 produces. You can describe this waveform as a constant-voltage source in any commercial Spice program, such as Intusoft's (www.intusoft.com) Model ICAP/4Rx V8.8.1. You enter V1's parameters as manual-driven inputs, and this Spice program automatically generates the following statement for V1: V1 12 0 PULSE 4 8 0 11.1E-6 11.1E-6 1E-12 22.2E-6, where "12 0" designates the two nodes for V1.

The MOSFET on-resistance of 0.25Ω determines the values of R1, R2, R3, and R4. The addition of Rq=600Ω and Vcc=12V model the SA50 amplifier's quiescent current and the low-voltage power supply necessary to power the H-bridge drive circuitry.


Figure 5 shows the complete Spice subcircuit for the SA50. This basic SA50 can drive a bidirectional motor for which Vin controls the motor speed and direction of rotation. You can add LC filters that let you drive other loads. Even when driving a motor, LC filters next to the amplifier module are useful for EMI and EMC purposes. Without filters, the long cables to the motor carry high-voltage switching pulses and act as antennas. Because the waveform across AOUT and BOUT is a pulse train of variable duty cycle and because Vin, the analog input signal, controls the pulse train's duty cycle or pulse width, you must first filter the PWM pulse train to extract the analog output signal.

In Figure 5, the load comprises Rload and Lload. L1, C4, L3, and C5 form a lowpass filter with a cutoff frequency (Fc) of 4.5 kHz to filter out the SA50 amplifier's 45-kHz PWM pulse train. A rule of thumb is to set the LC filter's corner frequency one decade below the PWM frequency. Of course, you can push the corner frequency higher by using multiple-pole LC filters. The equations to calculate filter LC values are as follows:

$$L1 = L3 = \frac{1.4142 \times R_{load}}{2\pi \times F_c} \times 0.5, \quad (1)$$


$$C4 = C5 = \frac{0.7071}{2\pi \times F_c \times R_{load}} \times 2. \quad (2)$$

FIGURE 6

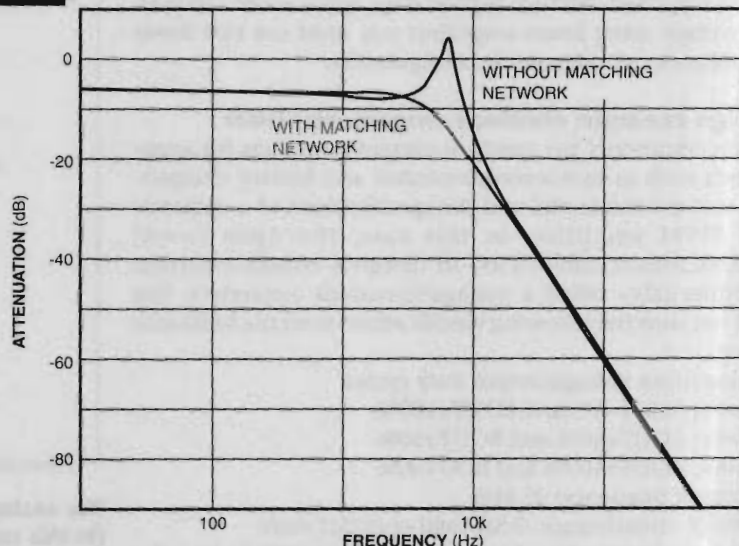

The LC filter's frequency response differs with and without the matching network.

FIGURE 7

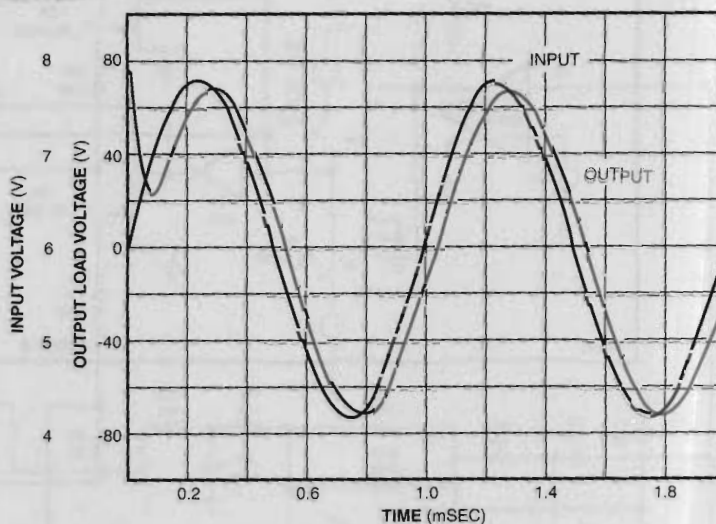

Ignoring the feedback circuitry of X3 and X4, a 1-kHz, 3.5V p-p sine wave with offset at Vin produces a 120V p-p sine wave across the load.

Because of the filter's differential configuration, these equations include a $\times 0.5$ factor for L1 and L3 and a $\times 2$ factor for C4 and C5. In this example, Rload=16Ω, and Fc=4.5 kHz, so L1=L3=400 μH, and C4=C5=3.1 μF. Because the load for this example is inductive, adding the matching network of R17 and C8 creates a combined load of 16Ω. The equations for R17 and C8 are as follows:

PWM AMPLIFIERS

$$R_{17} = R_{load},$$

$$C8 = \frac{L_{load}}{R_{load}^2}.$$

In this example, $L_{load}=1\text{ mH}$, and $R_{load}=16\Omega$, so $C_8=3.9\text{ }\mu\text{F}$, and $R_{17}=16\Omega$. Similarly, if you have a capacitive load, you can use a LC matching network to make the combined load resistive, for which

$$L = C_{load} \times R_{load}^2. \quad (5)$$

Figure 6 shows the frequency response of the filter with and without the matching network. Ignoring the feedback circuitry of X3 and X4, a 1-kHz 3.5V p-p sine wave with 6V-dc offset at Vin produces a 120V p-p sine wave across the load (Figure 7).

To complete the design of a constant-current amplifier,

(3) you must have some means of sensing the load current and provide feedback control in case of a load change. R_a and R_b are the two current-sensing resistors. Op amp X4 and its associated components serve two purposes: first, as a difference amplifier with a gain of 20 that converts the current difference between R_a and R_b into a voltage output of $-0.5A/V$ and, second, as a lowpass filter comprising C1, C2, C6, and C7 that filters the ripple currents in R_a and R_b with a corner frequency of 4.5 kHz. The design equations are as follows:

$$\text{GAIN} = -\frac{R_9}{R_{10} \times R_a} A/V, \quad (6)$$

$$C6 = C7 = \frac{1}{2\pi \times R13 \times Fc}, \quad (7)$$

$$C1 = C2 = \frac{1}{2\pi \times R10 \times Fc}. \quad (8)$$

LISTING 1-PWM CONSTANT-CURRENT-AMPLIFIER SPICE CIRCUIT

```
*NAME V(1) V(2S) 2R4(i) 2R4(p) 2R1(i) 2R1(p) V(9)
**NAME V(2S) 2R3(i) 2R3(p) V(7) V(2S) 2R2(i) 2R2(p) V(9)
**NAME 2V(i) 2V(p) V(10) 2S4(i) 2S4(p) V(11) 2S2(i) 2S2(p)
**NAME 2S3(i) 2S3(p) 2S1(i) 2S1(p) V(12) 2V1(i) 2V1(p) V(13)
**NAME V(18) 2S4(i) 2S1(p) 2V5(i) 2V5(p) V(8) 2S6(i) 2S6(p)
**NAME V26(i) 2V6(p) V(17) 2RLoad(i) 2RLoad(p) 2LRB(i) 2LRB(p)
**NAME 2RA(i) 2RA(p) V(16) V(14) V(20) V(21) 2RR(i) 2RR(p)
**NAME 2R9(i) 2R9(p) 2R10(i) 2R10(p) 2R11(i) 2R11(p) 2V3(i) 2V3(p)
**NAME 2C1(i) 2C2(i) V(24) V(18) V(26) 2R12(i) 2R12(p) 2VEIN(i)
**NAME 2VEIN(p) 2C3(i) 2R14(i) 2R14(p) 2S5(i) 2S5(p) V(15) V(30)
**NAME V(21) 2L1(i) 2L1(p) 2C4(i) 2C4(p) 2R13(i) 2R13(p) 2C6(i)
**NAME 2R15(i) 2R15(p) 2C7(i) V(23) V(29) V(6) V(4) V(21)
**NAME V(22) 2V2(i) 2V2(p) V(27) 2Vao(i) 2Vcp(i) 2Rq(i) 2Rq(p)
**NAME V(28) 2R17(i) 2R17(p) 2C8(i) 2RLoad(i)
*VIEW TRAN Yz
*alias Y1 2RLoad(i)
TRAN 22.2E-9 4000E-6 0 22.2E-8 UIC
.PRINT TRAN Yz
R4 1 25 0.25
R1 3 23 0.25
R3 9 29 0.25
R2 7 19 0.25
V4 9 0 DC=80
S4 29 1 10 0 S4 mod
.MODEL S4 mod SW VT=2.5 RCON=1E-9 ROFF=1E9
S2 29 7 11 0 S2 mod
.MODEL S2 mod SW VT=2.5 RCON=1E-9 ROFF=1E9
S3 9 5 11 0 S3 mod
.MODEL S3 mod SW VT=2.5 RCON=1E-9 ROFF=1E9
S1 3 9 10 0 S1 mod
.MODEL S1 mod SW VT=2.5 RCON=1E-9 ROFF=1E9
X1 11 10 INJ 1
.SUBCKT INJ 1 2
* in out
B1 3 0 V=-V(1)
CD 3 2 1
RD 2 0 .87NF
.ENDS
V1 12 0 PULSE 4 9 0 11.1E-6 11.1E-6 1E-12 22.2E-6
E1 13 0 12 18 1E9
**NAME 2G1(i) 2G1(p)
L1 23 4 400u
V5 18 0 DC=5
S6 11 9 0 13 S6 mod
.MODEL S6 mod SW VT=2.5 RCON=1E-9 ROFF=1E9
V6 0 8 EC=5
ALoad 17 6 16
V2 0 22 DC=12
Lload 4 17 1m
PD 25 0 0.1
Ra 19 0 0.1
K3 16 14 20 21 22 PA21 ( )
.SUBCIR PA21 1 2 3 4 5
* PRINT ORDER +IN -IN OUT +V -V
Q1 10 1 8 Q11
Q2 11 2 9 Q12
R3 12 4 7.38E+03
R4 12 9 7.38E+03
I2 4 9 3.61E-08
C1 12 5 2.73E-12
R5 13 5 1.1E+06
C1 12 5 2.73E+03
R2 4 11 8.85E+03
C2 10 14 9.00E-12
I1 4 9 3.76E-02
W1 6 15 4 10 1.13E-04
G2 6 14 12 18 6.36E-09
R6 6 15 1.40E+09
H4 9 13 DD
D2 14 6 DD
C3 6 7 3.00E-11
G3 15 7 15 6 8.85E+00
R7 7 15 1E3
D3 7 16 DD
V1 18 16 1.60E+00
D4 17 7 DD
V2 17 19 1.60E+00
REL 15 0 0.001
EZ 18 0 4 0 1
G3 19 0 5 0 1
R8 7 20 50
C4 20 15 3.08E-09
Q3 19 20 21 GOP
C4 19 20 22 GON
Q5 4 23 29 GON
O6 5 24 30 GOP
Q7 25 27 31 OLN
Q8 26 28 31 QLP
R11 21 23 1.70E-01
RCLEP 29 31 1.70E-01
RCLN 30 31 1.70E-01
R13 22 24 1.70E-01
D5 23 25 DL
D6 26 24 DL
R9 27 29 1E3
R10 28 30 1E3
I3 18 23 7.92E-03
I4 24 19 7.92E-03
R15 31 3 5.42E-01
RSN 3 34 1
CSN 34 5 0.1E-6
.MODEL DD D(CJO)=0.1PF IS=1E-17)
.MODEL DL D(CJO)=3PF IS=1E-13)
.MODEL Q11 NPN (BF=4.55E+02 IS=1E-16)
.MODEL Q12 NPN (BF=4.24E+02 IS=1.46E-16)
.MODEL GOP PNP (BF=4.64E+02 IS=1E-14)
.MODEL GON PNP (BF=4.64E+02 IS=1E-14)
.MODEL QLN NPN (BF=100 IS=1E-14)
.MODEL QLP PNP (BF=100 IS=1E-14)
.ENDS
R8 16 30 10K
R9 14 2 10K
R10 14 20 200K
R11 16 0 200K
Vcc 27 0 DC=12
V3 21 0 DC=12
C1 16 0 180p
C2 14 20 180p
RG 27 0 600
X3 0 24 18 21 22 PA21 ( )
R12 24 26 10K
VEIN 26 0 DC=10
C3 18 24 71n
S5 15 11 13 0 S5 mod
.MODEL S5 mod SW VT=2.5 RCON=1E-9 ROFF=1E9
L3 29 6 400u
R14 24 20 10K
C4 0 4 3.1u
C5 0 6 3.1u
R17 28 6 16
R13 30 25 100
C6 30 0 0.35u
C8 4 28 3.5u
R15 2 19 100
C7 2 0 0.35u
.END
```

PWM AMPLIFIERS

To minimize power losses, you should choose R_a and R_b values of 0.01 to 0.1 Ω . In this example, $F_c=4.5$ kHz. $R_8=R_9=10$ k Ω . To minimize loading effects, these resistors must be much greater than $R_{13}=R_{15}=100\Omega$. Substituting these values into Equation 7 and Equation 8, $C_6=C_7=0.35$ μ F, and $C_1=C_2=180$ pF. Choosing $R_{10}=200$ k Ω , Equation 6 yields a gain of -0.5 A/V.

X3 is an integrator that compares the error voltage from X4 with the input voltage E_{in} and provides the correct input voltage for the SA50 amplifier to close the feedback loop. The design equations for the integrator are as follows:

$$R_{12} = R_{14}, \quad (9)$$

$$C_3 = \frac{1}{2\pi \times (0.05F_c) \times R_{12}}. \quad (10)$$

You can complete the design by choosing $R_{12}=R_{14}=10$ k Ω and $C_3=71$ nF (Figure 6).

You can now run the Spice program. The load current waveforms (Figure 8) are as expected. Note that there is a small error between the Spice output and the expected value.

For example, with $E_{in}=10$ V, the expected output current should be -5 A, but Figure 8 shows -4.8 A. This difference is because of the loss resulting from the 0.25 Ω MOSFET's on-resistance. If you set the on-resistance to zero, you get exactly -5 A. Listing 1 is the complete Spice circuit description for the constant-current amplifier.

Constant-voltage amplifier

In applications such as audio-speaker drivers, motor-speed control, and power inverters, you need a constant voltage amplifier. You can use the Apex SA02 to design a high-efficiency, high-power PWM audio-speaker driver. The SA02 data sheet lists the following specifications:


Analog input voltage/output duty cycles:

$V_{in}=1.25$ V; AOUT=0%, BOUT=100% $V_{in}=2.50$ V; AOUT=50%, BOUT=50% $V_{in}=3.75$ V; AOUT=100%, BOUT=0% switching frequency: 250-kHz

MOSFET on-resistance: 0.42 Ω total or 0.21 Ω each.

The LC filter design is similar to that of the constant-current amplifier except the LC filter requires no matching network because of the 8 Ω resistive load (Figure 9a). The SA02 amplifier's PWM frequency is 250 kHz, so the design sets the

FIGURE 9


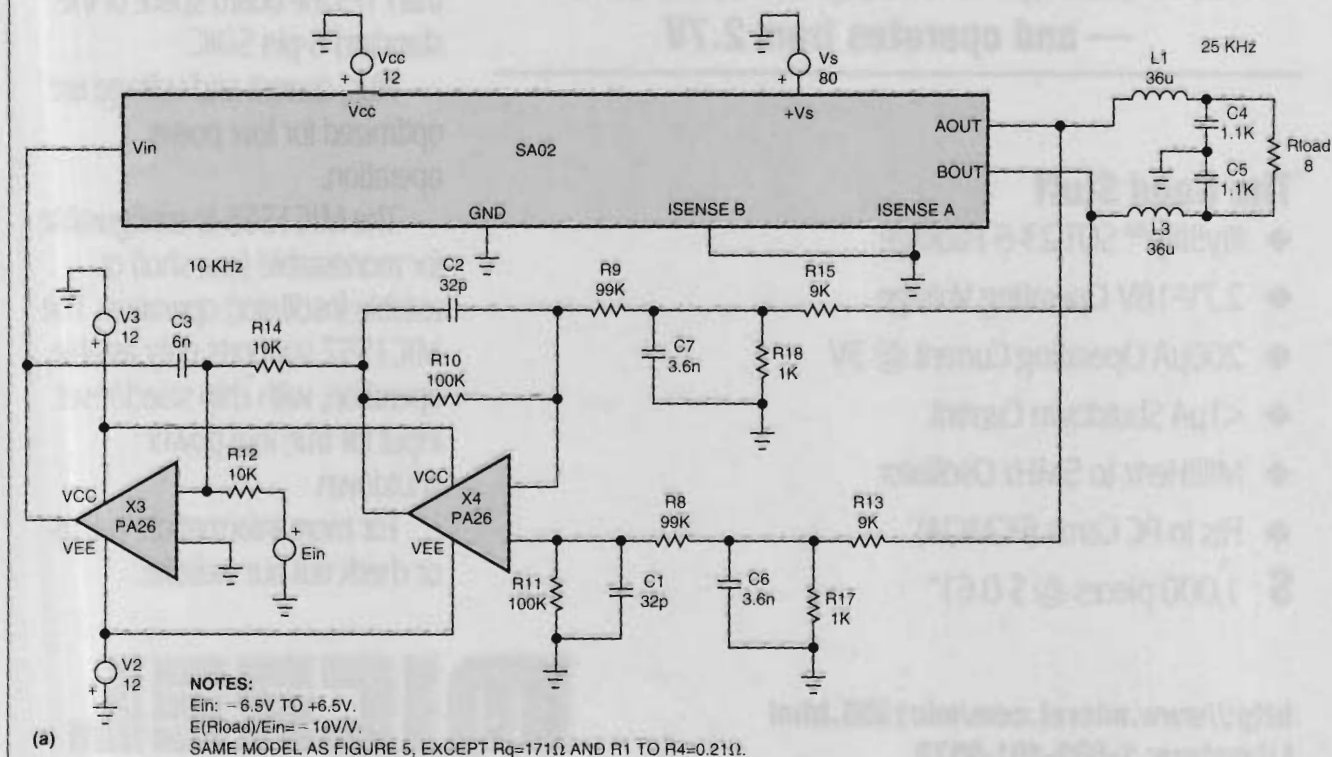


A similar model using specifications from the SA02 amplifier is part of a constant-voltage feedback amplifier (a). The output sine wave takes about 50 μ sec to stabilize (b).

LC filter's corner frequency to 25 kHz. The design of the difference amplifier (X4) is somewhat different, however. This constant-voltage amplifier configuration senses the output voltage, not the output current. The voltage at AOUT and BOUT is much higher than the voltage across the current-sensing resistors in the previous example. Instead of boosting the gain, resistor dividers lower the sense voltage to levels that a small signal amplifier can handle. The integrator's (X3) time constant is faster to provide the frequency response necessary for audio applications. The SA02 audio-speaker driver has a -10V/V voltage gain and a 10-kHz

Spice-simulation runs indicate the load-current waveforms of the constant-current amplifier for various values of E_{in} .

FIGURE 8

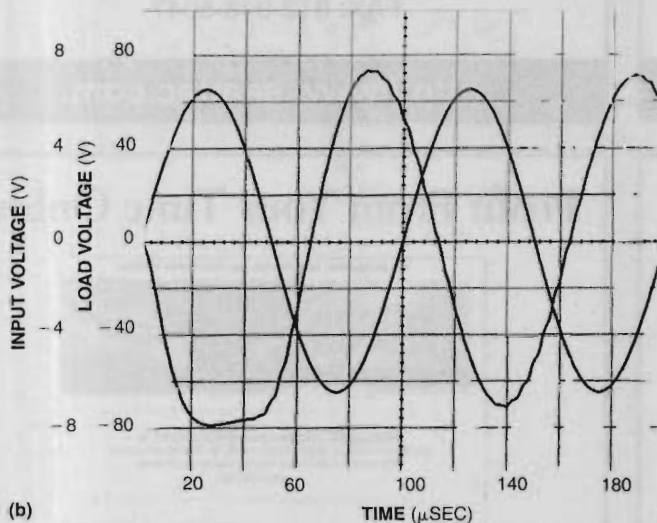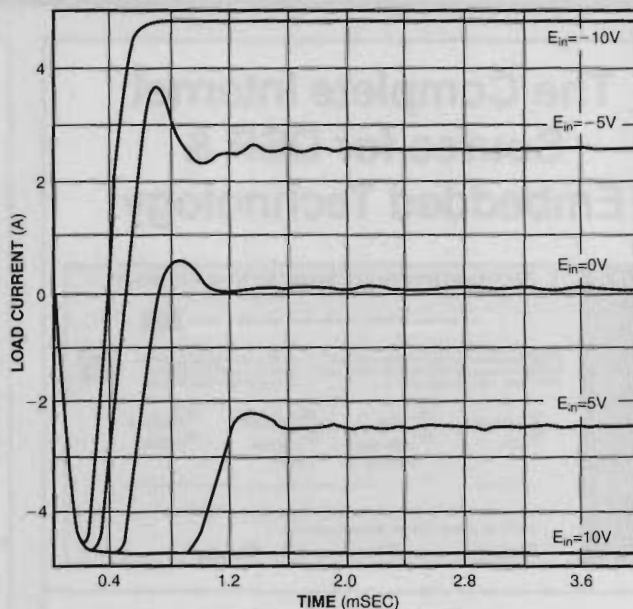

power bandwidth. Figure 9b shows the circuit's input and output waveforms. Note that it takes about 50 μsec for the output's sine wave to stabilize.

The SA02 has many bells and whistles, such as thermal sensing and external-logic shut-down, that the generic model does not implement. A design engineer can easily analyze these independent features with a paper and pencil. However, this simple yet versatile model makes it easy to model the main PWM function when manual analysis of this feedback-control circuit becomes unmanageable.

EDN

Author's biography

Yu Jen Wong is an application engineer at Apex Microtechnology Corp (www.apexmicrotech.com), where he has worked for four years. He works with system engineers to design power amplifiers in applications such as motion control, automated test equipment, deflection, and piezo drivers. Wong holds a BSEE from the University of Hong Kong and an MSEE from the University of Tennessee.

VOTE

Please use the Information Retrieval Service card to rate this article (circle one):

High Interest	Medium Interest	Low Interest
582	583	584